

EE-18 Exam 2
Fall, 2003
Prof. Traver

Name: _____ Key _____

1. Write a VHDL concurrent statement to implement the Boolean function:

$$P = (AB' + C)(B \oplus D)$$

```
P <= ((A and NOT B) OR C) AND (B XOR D);
```

2. Draw the logic circuit that is described by the following structural VHDL description.

```
entity circuit is
port ( X, Y, Z : in bit; F, G: out bit);
end circuit;

architecture exam_problem of circuit is

component AND is
port (A,B: in bit; C out bit);
end component;


component OR is
port (A,B: in bit; C out bit);
end component;

signal S1, S2 : bit;

begin

G1: AND port map (X, Y, S1);
G2: AND port map (Y, Z, S2);
G3: OR port map (S1, S2, F);
G4: AND port map (S1, Z, G);


end exam_problem;
```

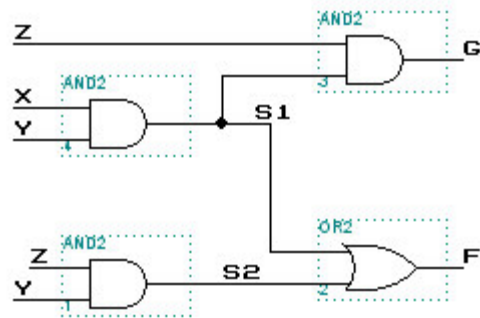


5. Use the multiplexor shown to implement the function F.

$$F(a,b,c) = \sum m(0,4,5,7)$$

a	b	c	F	
0	0	0	1	F=c'
0	0	1	0	
0	1	0	0	F=0
0	1	1	0	
1	0	0	1	F=1
1	0	1	1	
1	1	0	0	F=c
1	1	1	1	

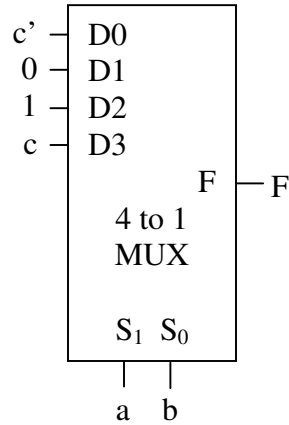

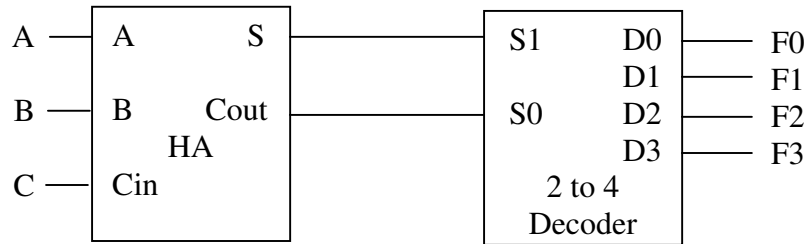6. In the circuit below, a Half-Adder (HA) circuit is connected to a 2 to 4 decoder. Fill in the resulting function table for the overall circuit.



A	B	C	F0	F1	F2	F3
0	0	0	1	0	0	0
0	0	1	0	0	1	0
0	1	0	0	0	1	0
0	1	1	0	1	0	0
1	0	0	0	0	1	0
1	0	1	0	1	0	0
1	1	0	0	1	0	0
1	1	1	0	0	0	1

7. Perform the following subtraction by translating to binary (8-bits), and applying the 2's complement approach.

$$96 - 73$$

$$96 = 01100000$$



$$73 = 01001001$$

$$-73 = 10110111$$

$$96 - 73 = 96 + (-73)$$

$$\begin{array}{r} 01100000 \\ +10110111 \\ \hline 1\ 00010111 = 23 \end{array}$$

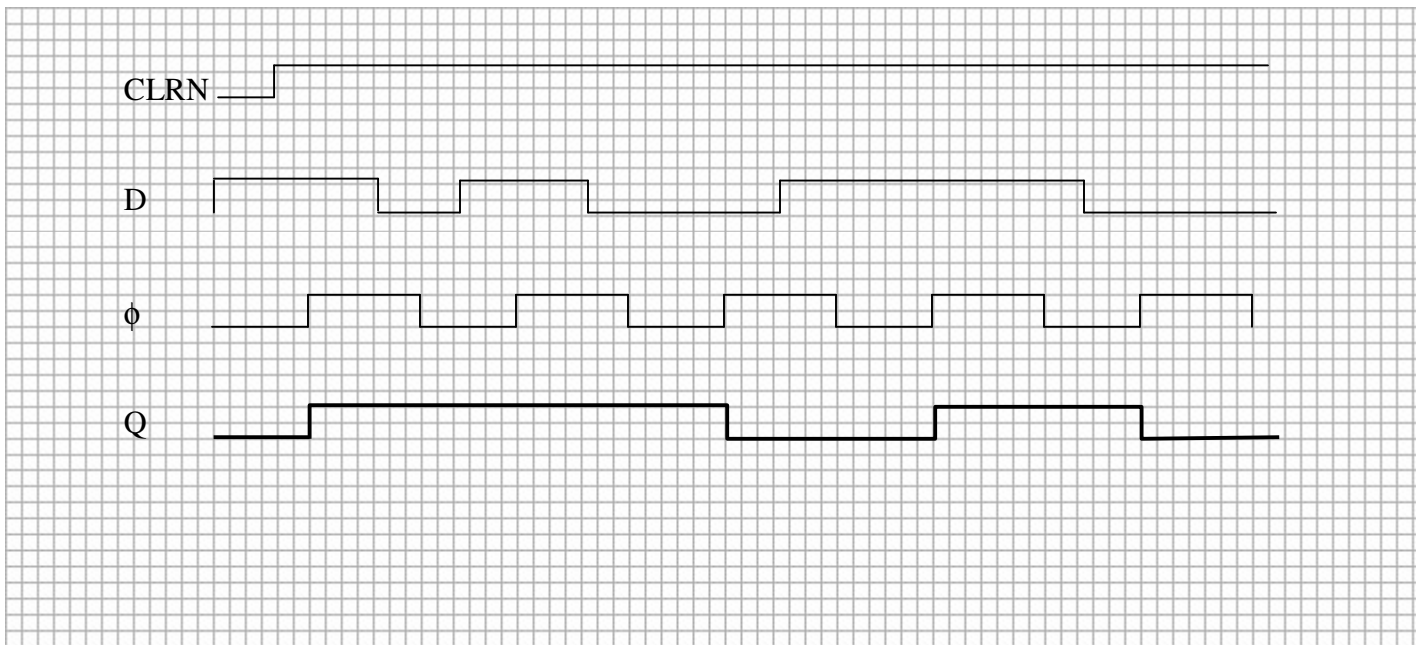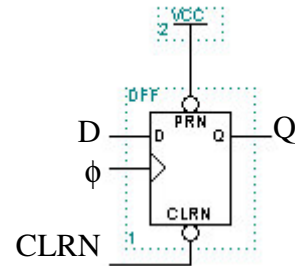8. Fill in the waveform for the output of the flip-flop shown.



9. An 8-bit register is initially loaded with the value 01101101. Give the contents of the register (in binary) after the following operations are performed:

a) ROL 3

01101011

b) SHL 2

10110100

c) ROR 1

10110110

10. Given a RAM module of size 512 x 8.

a) How many address lines does it have?

$$512 = 2^9$$

Therefore, 9 address lines

b) How many data lines does it have?

8

c) How many of these 512 x 8 RAMs are needed to build a 1K x 16 RAM?

For correct number of bits per word, expand horizontally by 2

For correct number of words, expand vertically by 2

Therefore, we need 4 of the 512 x 8 RAMS to make a 1K x 16 RAM.